

# Oplæg til øvelse Calculator

Det anbefales at man nøjes med en binær (hex) version – BCD funktionen kan vente

Op(4:0) = 0 0 0 0 0 = Binær =>

Op(4:0) = 0 0 0 0 1 = BCD =>

Op(4:0) = 1 0 0 0 0 = + =>

Op(4:0) = 1 0 0 0 1 = + BCD =>

Op(4:0) = 0 1 0 0 0 = - =>

Op(4:0) = 0 1 0 0 1 = - BCD =>

Op(4:0) = 0 0 1 0 0 = \* =>

Op(4:0) = 0 0 1 0 1 = \* BCD =>

Op(4:0) = 0 0 0 1 0 = / =>

Op(4:0) = 0 0 0 1 1 = / BCD =>

Disp(3:2)

a

BCD(a)

Disp(1:0)

b

BCD(b)

a+b

BCD ( a+b)

a-b

BCD ( a-b)

a\*b

BCD ( a\*b)


a/b

BCD(a/b)

a MOD b

BCD(a MOD b)

 Brug evt. dp til mest  
betydende cifre i  
forbindelse med BCD



Brug eventuelt  
Lysdioder også

Design Sources (1)


Calculator\_toplevel(Behavioral) (Calculator\_toplevel.vhd) (3)

U1: MuxDisplay3(Version3) (MuxDisplay3.vhd)

U2: calculator(Version3) (calculator\_IP.vhd)

U3: bin2BCDx(Behavioral) (bin2BCDx.vhd)
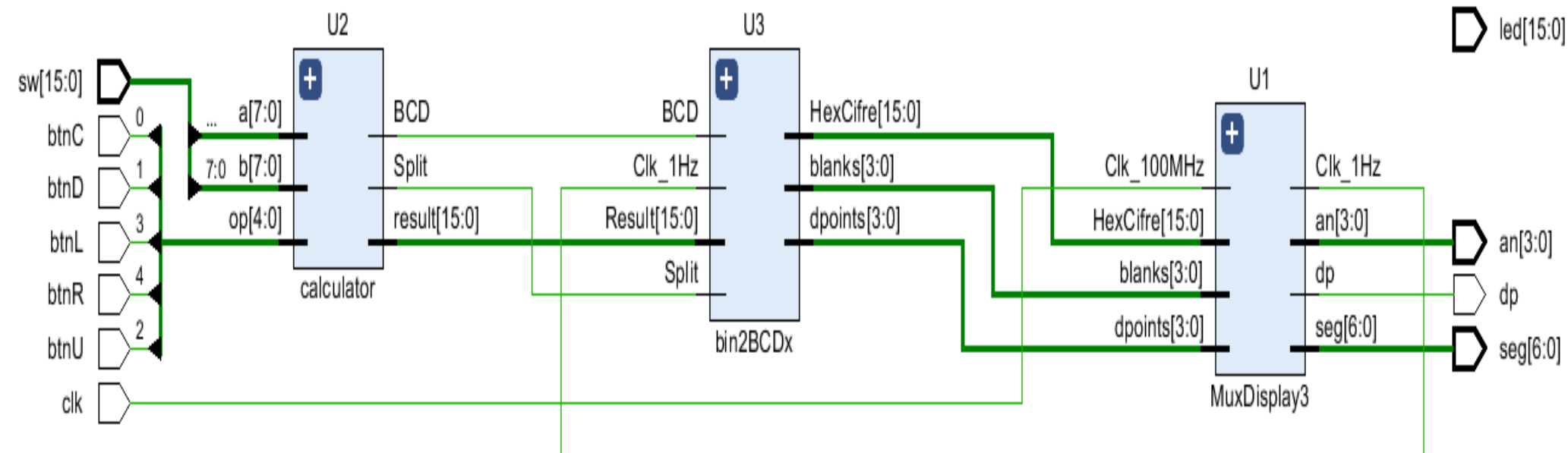
```
entity Calculator_toplevel is
    Port ( clk : in STD_LOGIC;
          sw : in STD_LOGIC_VECTOR (15 downto 0);
          btnL,btnR,btnC,btnU,btnD : in STD_LOGIC;
          led : out STD_LOGIC_VECTOR (15 downto 0);
          seg : out STD_LOGIC_VECTOR (6 downto 0);
          dp : out STD_LOGIC;
          an : out STD_LOGIC_VECTOR (3 downto 0));
end Calculator_toplevel;
```



```

architecture Behavioral of Calculator_toplevel is
    component MuxDisplay3
        port (Clk_100MHz : in std_logic;
              HexCifre  : in std_logic_vector (15 downto 0);
              dpoints   : in std_logic_vector (3 downto 0);
              blanks    : in std_logic_vector (3 downto 0);
              Clk_1kHz  : out std_logic;
              Clk_1Hz   : out std_logic;
              an        : out std_logic_vector (3 downto 0);
              seg       : out std_logic_vector (6 downto 0);
              dp        : out std_logic);
    end component;

    signal HexCifre : std_logic_vector (15 downto 0);
    signal dpoints  : std_logic_vector (3 downto 0);
    signal blanks   : std_logic_vector (3 downto 0);
    signal Clk_1kHz : std_logic;
    signal Clk_1Hz  : std_logic;

    component calculator
        port (a      : in std_logic_vector (7 downto 0);
              b      : in std_logic_vector (7 downto 0);
              op     : in std_logic_vector (4 downto 0);
              BCD    : out std_logic;
              Split  : out std_logic;
              result : out std_logic_vector (15 downto 0));
    end component;

    signal a      : std_logic_vector (7 downto 0);
    signal b      : std_logic_vector (7 downto 0);
    signal op     : std_logic_vector (4 downto 0);
    signal BCD    : std_logic;
    signal Split  : std_logic;
    signal result : std_logic_vector (15 downto 0);

    component bin2BCDx
        port (Split : in std_logic;
              Result : in std_logic_vector (15 downto 0);
              BCD    : in std_logic;
              Clk_1Hz : in std_logic;
              HexCifre : out std_logic_vector (15 downto 0);
              dpoints : out std_logic_vector (3 downto 0);
              blanks  : out std_logic_vector (3 downto 0));
    end component;
end architecture Behavioral;

```

```

begin
    op <= btnR & btnL & btnU & btnD & btnC;

    U1 : MuxDisplay3
        port map (Clk_100MHz => clk,
                  HexCifre  => HexCifre,
                  dpoints   => dpoints,
                  blanks    => blanks,
                  Clk_1kHz  => Clk_1kHz,
                  Clk_1Hz   => Clk_1Hz,
                  an        => an,
                  seg       => seg,
                  dp        => dp);

    U2 : calculator
        port map (a      => sw(15 downto 8),
                  b      => sw( 7 downto 0),
                  op     => op,
                  BCD    => BCD,
                  Split  => Split,
                  result => Result);

    U3 : bin2BCDx
        port map (Split  => Split,
                  Result  => Result,
                  BCD     => BCD,
                  Clk_1Hz => Clk_1Hz,
                  HexCifre => HexCifre,
                  dpoints => dpoints,
                  blanks  => blanks);
end Behavioral;

```

ENTITY MuxDisplay3 is

Port (Clk\_100MHz: in STD\_LOGIC;

HexCifre: in STD\_LOGIC\_VECTOR (15 downto 0);

dpoints: in STD\_LOGIC\_VECTOR (3 downto 0);

blanks: in STD\_LOGIC\_VECTOR (3 downto 0);

Clk\_1kHz: out STD\_LOGIC;

Clk\_1Hz: out STD\_LOGIC;

an: out STD\_LOGIC\_VECTOR (3 downto 0);

seg: out STD\_LOGIC\_VECTOR (6 downto 0);

dp: out STD\_LOGIC);

end MuxDisplay3;

ARCHITECTURE Version3 of MuxDisplay3 is

BEGIN

Mux\_Display3:

process( Clk\_100MHz,HexCifre,blanks,dpoints)

variable Scale100000: integer range 0 to 100000;

variable Scale1023: std\_logic\_vector( 9 downto 0);

variable X: std\_logic\_vector( 1 downto 0) := "00";

variable Xi: integer range 0 to 3;

variable HexDig: std\_logic\_vector( 3 downto 0);

type ROM\_array is array (0 to 15) of std\_logic\_vector (1 to 7);

constant Hex27Segm: ROM\_array := (

"1000000","1111001","0100100","0110000", -- 0123

"0011001","0010010","0000010","1111000", -- 4567

"0000000","0010000","0001000","0000011", -- 89Ab

"1000110","0100001","0000110","0001110");-- CdEF

begin

begin

----- Sequential logic

if rising\_edge( Clk\_100MHz) then

if Scale100000 <100000 then

Scale100000 := Scale100000+ 1;

Clk\_1kHz <= '0';

else

Scale100000 := 1;

Clk\_1kHz <= '1';

Scale1023 := Scale1023+1;

-- Clk\_1Hz <= Scale1023(9) or Scale1023(8); -- 75% Duty cycle

Clk\_1Hz <= Scale1023(9); -- approx. 1 Hz 50% Duty cycle

X := X+1;

Xi := conv\_integer(X);

end if;

end if;

----- Combinatorial logic

-- Note! HexCifre and dpoints must now be added to the sensivity list

HexDig := HexCifre( Xi\*4+3 downto Xi\*4);

if Blanks(Xi)='1' then

seg <= "1111111";

dp <= '1';

else

seg <= Hex27Segm( Conv\_integer(HexDig));

dp <= not dpoints(Xi);

end if;

an <= "1111";

an(Xi) <= '0';

end process;

end Version3;

```

entity bin2BCDx is
    Port ( Split :    in STD_LOGIC;
          Result :    in STD_LOGIC_VECTOR (15 downto 0);
          BCD :      in STD_LOGIC;
          Clk_1Hz :   in STD_LOGIC;
          HexCifre :  out STD_LOGIC_VECTOR (15 downto 0);
          dpoints :   out STD_LOGIC_VECTOR (3 downto 0);
          blanks :    out STD_LOGIC_VECTOR (3 downto 0)
    );
end bin2BCDx;

```


```

architecture Behavioral of bin2BCDx is
    signal ax:      STD_LOGIC_VECTOR (7 downto 0);
    signal bx:      STD_LOGIC_VECTOR (7 downto 0);
    signal rx:      STD_LOGIC_VECTOR (15 downto 0);

    signal aBCD:    STD_LOGIC_VECTOR (11 downto 0);
    signal bBCD:    STD_LOGIC_VECTOR (11 downto 0);
    signal rBCD:    STD_LOGIC_VECTOR (19 downto 0);

begin
    ax <= Result( 15 downto 8);
    bx <= Result( 7  downto 0);
    rx <= Result;

```

 



architecture Behavioral of bin2BCDx is

```
    signal ax:      STD_LOGIC_VECTOR (7 downto 0);  
    signal bx:      STD_LOGIC_VECTOR (7 downto 0);  
    signal rx:      STD_LOGIC_VECTOR (15 downto 0);
```

```
    signal aBCD:    STD_LOGIC_VECTOR (11 downto 0);  
    signal bBCD:    STD_LOGIC_VECTOR (11 downto 0);  
    signal rBCD:    STD_LOGIC_VECTOR (19 downto 0);
```

begin

```
    ax <= Result( 15 downto 8);  
    bx <= Result( 7  downto 0);  
    rx <= Result;
```

BCD\_a: process(ax)

```
    variable bcd_data : integer;  
    variable huns_data: integer;  
    variable tens_data: integer;  
    variable ones_data: integer;
```

begin

```
    bcd_data := conv_integer(ax);  
    ones_data := bcd_data mod 10;  
    bcd_data := bcd_data / 10;  
    tens_data := bcd_data mod 10;  
    huns_data := bcd_data / 10;
```

```
    aBCD(11 downto 8) <= conv_std_logic_vector(huns_data,4);  
    aBCD( 7 downto 4) <= conv_std_logic_vector(tens_data,4);  
    aBCD( 3 downto 0) <= conv_std_logic_vector(ones_data,4);
```

end process;

BCD\_b: process(bx)

```
    variable bcd_data : integer;  
    variable huns_data: integer;  
    variable tens_data: integer;  
    variable ones_data: integer;
```

begin

```
    bcd_data := conv_integer(bx);  
    huns_data := bcd_data / 100;  
    bcd_data := bcd_data mod 100;  
    tens_data := bcd_data / 10;  
    bcd_data := bcd_data mod 10;  
    ones_data := bcd_data;
```

```
    bBCD(11 downto 8) <= conv_std_logic_vector(huns_data,4);  
    bBCD( 7 downto 4) <= conv_std_logic_vector(tens_data,4);  
    bBCD( 3 downto 0) <= conv_std_logic_vector(ones_data,4);
```

end process;

```

BCD_r: process(rx)
    variable bcd_data : integer;
    variable th10_data: integer;
    variable thos_data: integer;
    variable huns_data: integer;
    variable tens_data: integer;
    variable ones_data: integer;
begin
    bcd_data := conv_integer(rx);
    th10_data := bcd_data / 10000;
    bcd_data := bcd_data mod 10000;
    thos_data := bcd_data / 1000;
    bcd_data := bcd_data mod 1000;
    huns_data := bcd_data / 100;
    bcd_data := bcd_data mod 100;
    tens_data := bcd_data / 10;
    bcd_data := bcd_data mod 10;
    ones_data := bcd_data;

    rBCD(19 downto 16) <= conv_std_logic_vector(th10_data,4);
    rBCD(15 downto 12) <= conv_std_logic_vector(thos_data,4);
    rBCD(11 downto 8)  <= conv_std_logic_vector(huns_data,4);
    rBCD( 7 downto 4)  <= conv_std_logic_vector(tens_data,4);
    rBCD( 3 downto 0)  <= conv_std_logic_vector(ones_data,4);
end process;

```

```

architecture Behavioral of bin2BCDx is
    signal ax:      STD_LOGIC_VECTOR (7 downto 0);
    signal bx:      STD_LOGIC_VECTOR (7 downto 0);
    signal rx:      STD_LOGIC_VECTOR (15 downto 0);

    signal aBCD:    STD_LOGIC_VECTOR (11 downto 0);
    signal bBCD:    STD_LOGIC_VECTOR (11 downto 0);
    signal rBCD:    STD_LOGIC_VECTOR (19 downto 0);
begin
    ax <= Result( 15 downto 8);
    bx <= Result( 7  downto 0);
    rx <= Result;

```

```

Multiplekser: process( Result, BCD, Split)
begin
    HexCifre <= Result;
    dpoints  <= "0000";
    blanks   <= "0000";
    if BCD='1' then
        if Split='1' then
            HexCifre <= aBCD( 7 downto 0) & bBCD( 7 downto 0);
            dpoints  <= aBCD( 9) & aBCD( 8) & bBCD( 9) & bBCD(8);
            blanks   <= Clk_1Hz & Clk_1Hz & "00";
        else
            HexCifre <= rBCD( 15 downto 0);
            dpoints  <= rBCD( 19 downto 16);
            if rBCD(19 downto 4)="0000000000000000" then
                blanks <= "1110";
            elsif rBCD(19 downto 8)="000000000000" then
                blanks <= "1100";
            elsif rBCD(19 downto 12)="00000000" then
                blanks <= "1000";
            end if;
        end if;
    end if;
end process;

```

```

architecture Behavioral of bin2BCDx is
    signal ax:      STD_LOGIC_VECTOR (7 downto 0);
    signal bx:      STD_LOGIC_VECTOR (7 downto 0);
    signal rx:      STD_LOGIC_VECTOR (15 downto 0);

    signal aBCD:    STD_LOGIC_VECTOR (11 downto 0);
    signal bBCD:    STD_LOGIC_VECTOR (11 downto 0);
    signal rBCD:    STD_LOGIC_VECTOR (19 downto 0);
begin
    ax <= Result( 15 downto 8);
    bx <= Result( 7  downto 0);
    rx <= Result;

```

blink

aBCD=127  
bBCD=209  
split='1'



rBCD=971  
split='0'



blank



```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use ieee.numeric_std.all;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

ENTITY calculator is

```

Port ( a : in STD_LOGIC_VECTOR (7 downto 0);
      b : in STD_LOGIC_VECTOR (7 downto 0);
      op : in STD_LOGIC_VECTOR (4 downto 0); --> + - * / B
      BCD : out STD_LOGIC;
      Split : out STD_LOGIC;
      result : out STD_LOGIC_VECTOR (15 downto 0));

```

end calculator;

architecture Version3 of calculator is

```

    signal ax,bx: std_logic_vector(7 downto 0);

```

begin

```

    BCD <= op(0);

```

```

    ALU: process(a,b,op)

```

```

        variable ai, bi, ri: integer := 0;

```

```

    begin

```

```

        ai := conv_integer(a);

```

```

        bi := conv_integer(b);

```

```

        Split <= '0';

```

```

        case op(4 downto 1) is

```

```

            when "1000" =>

```

```

                ri := ai + bi;

```

```



                result <= conv_std_logic_vector(ri,16);

```

```

            when "0100" =>

```

 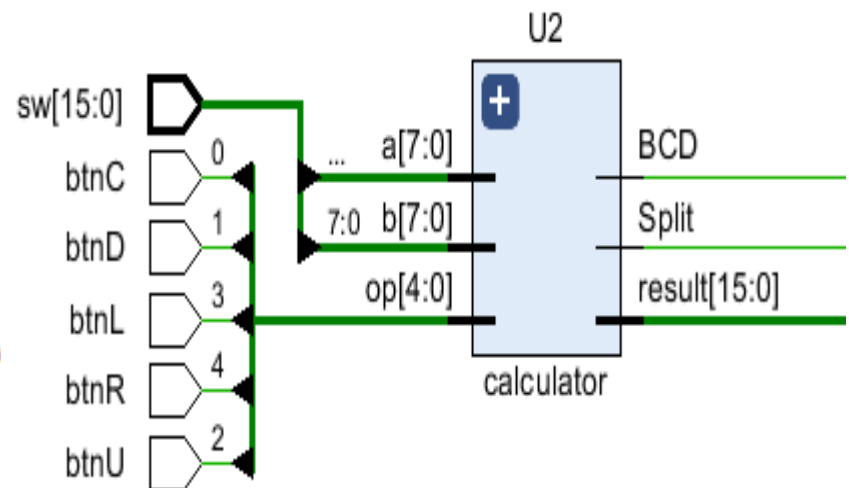

Løsning på næste side

```

architecture Version3 of calculator is
    signal ax,bx:      std_logic_vector(7 downto 0);
begin
    BCD <= op(0);

    ALU: process(a,b,op)
        variable ai, bi, ri: integer := 0;
    begin
        ai := conv_integer(a);
        bi := conv_integer(b);
        Split <= '0';
        case op(4 downto 1) is
            when "1000" =>
                ri := ai + bi;
                result <= conv_std_logic_vector(ri,16);
            when "0100" =>
                ri := ai - bi;
                result <= conv_std_logic_vector(ri,16);
            when "0010" =>
                ri := ai * bi;
                result <= conv_std_logic_vector(ri,16);
            when "0001" =>
                ax <= conv_std_logic_vector( ai/bi,8);
                bx <= conv_std_logic_vector( ai rem bi,8);
                result <= ax & bx;
                split <= '1';
            when others =>
                result <= a & b;
                split <= '1';
        end case;
    end process;
end Version3;

```